

KORTSLUTNINGS BEREGNING

- 3 typer kortslutninger
- Beregningseksempel
- Spændingsfaktor c



KELD DÝRMOSE




AAMS

Aarhus Maskinmesterskole
Aarhus School of Marine and Technical Engineering

3 typer kortslutninger


En stregs kredsskema:

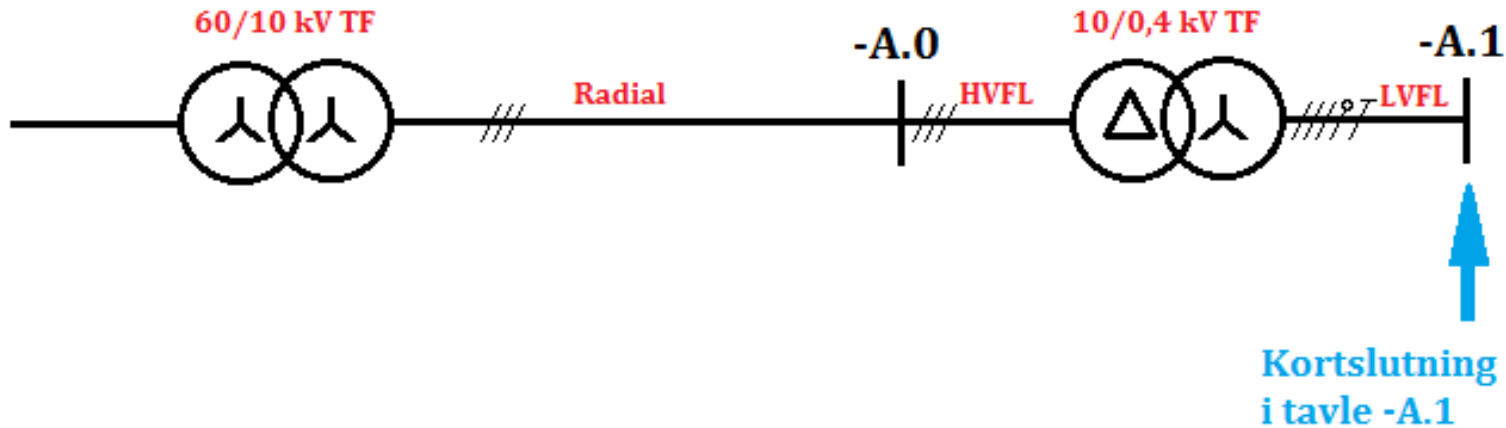

- 3 faset
- 2 faset
- 1 faset

3 faset kortslutning


Ækvivalent skema:

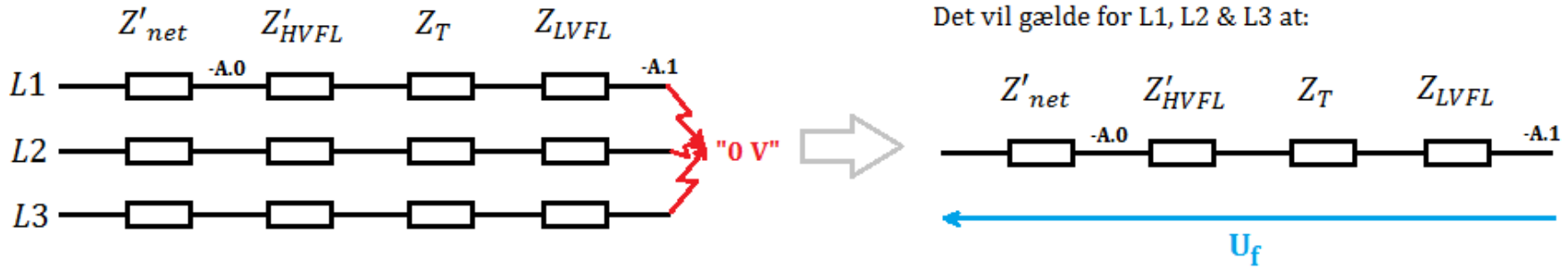

Beregning af den 3 fasede kortslutningsstrøm:

2 faset kortslutning


Ækvivalent skema:

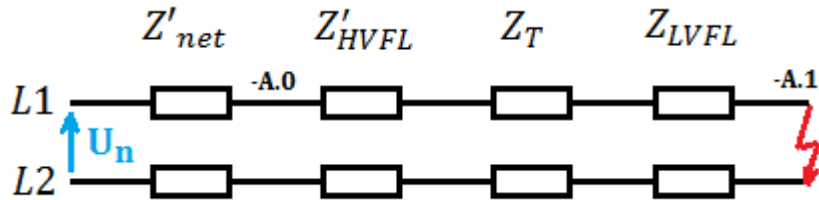

Beregning af den 2 fasede kortslutningsstrøm:

1 faset kortslutning


Ækvivalent skema:

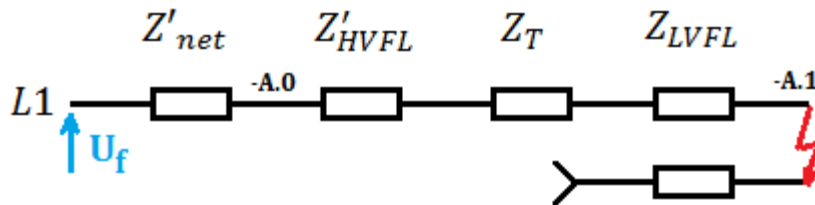

Beregning af den 1 fasede kortslutningsstrøm:

Beregningseksempel

En stregs skema:

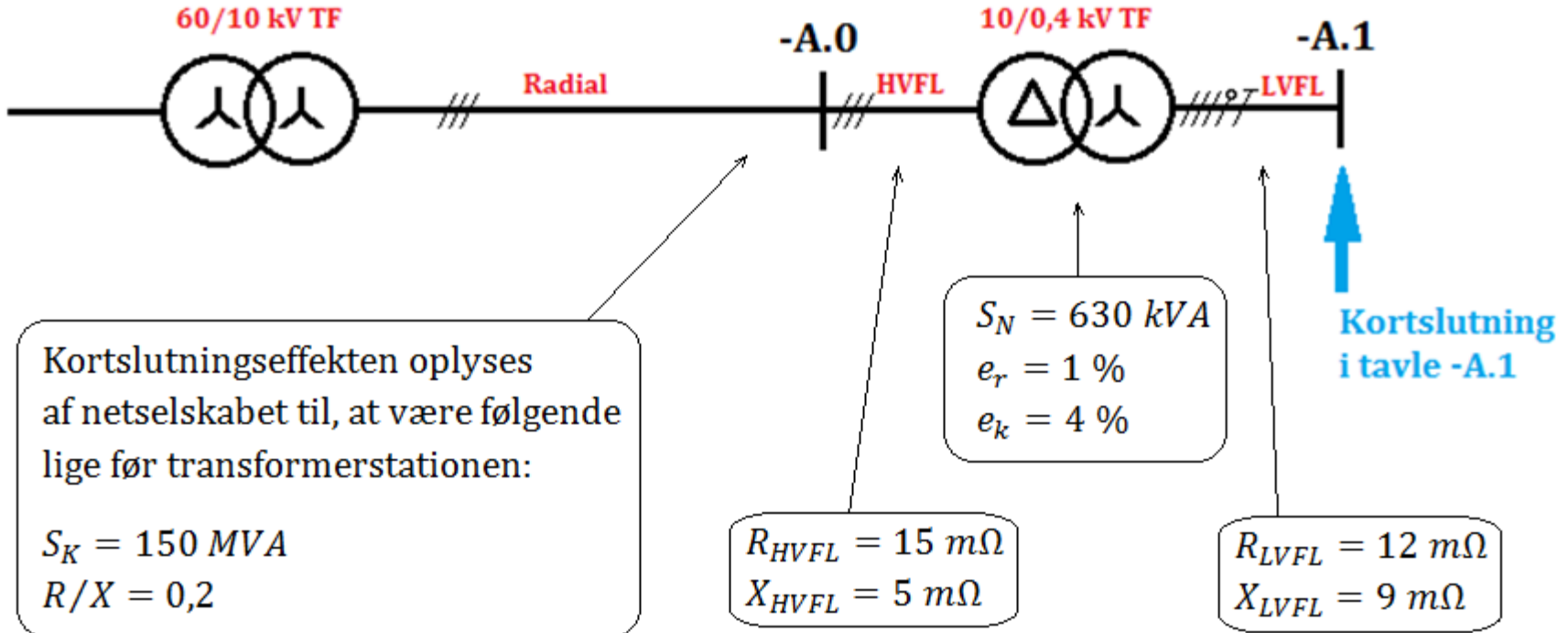

Netimpedans & transformerimpedans (Beregningseksempel)

Netimpedansen beregnes:

$$S_K = 150 \text{ MVA}$$


$$R/X = 0,2$$

Transformerimpedansen beregnes:

$$S_N = 630 \text{ kVA}$$

$$e_r = 1 \%$$

$$e_k = 4 \%$$

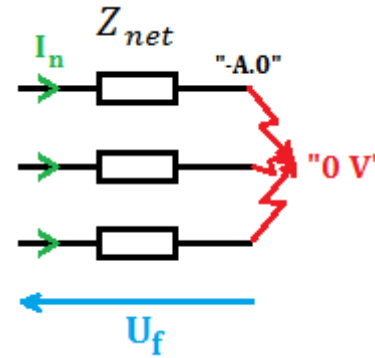

Netimpedansen:

$$S_K = 3 \cdot U_f \cdot I_n \Leftrightarrow$$

$$S_K = 3 \cdot \frac{U_n}{\sqrt{3}} \cdot I_n \Leftrightarrow$$

$$S_K = \sqrt{3} \cdot U_n \cdot I_n \Leftrightarrow$$

$$S_K = \sqrt{3} \cdot U_n \cdot \frac{U_f}{Z_{net}} \Leftrightarrow$$

$$S_K = \sqrt{3} \cdot U_n \cdot \frac{U_n}{\sqrt{3} \cdot Z_{net}} \Leftrightarrow$$

$$S_K = \frac{U_n^2}{Z_{net}} \Leftrightarrow$$

$$Z_{net} = \frac{U_n^2}{S_K}$$

Transformerimpedansen:

$$Z_T = \frac{U_f}{I_n} \cdot \frac{e_k}{100} \Leftrightarrow$$

$$Z_T = \frac{U_n}{\sqrt{3} \cdot I_n} \cdot \frac{e_k}{100} \Leftrightarrow$$

$$Z_T = \frac{U_n \cdot U_n}{\sqrt{3} \cdot I_n \cdot U_n} \cdot \frac{e_k}{100} \Leftrightarrow$$

$$Z_T = \frac{U_n^2 \cdot e_k}{S_N \cdot 100}$$

Henføring af impedanser (Beregningseksempel)

Vi har nu følgende impedanser:

$$Z_{net} = 0,667 \Omega \angle 78,7^\circ$$

$$R_{HVFL} = 15 \text{ m}\Omega$$

$$X_{HVFL} = 5 \text{ m}\Omega$$

$$Z_T = 10,2 \text{ m}\Omega \angle 75,5^\circ$$

$$R_{LVFL} = 12 \text{ m}\Omega$$

$$X_{LVFL} = 9 \text{ m}\Omega$$

Henføringsprincip:

$$n = \frac{U_{N1}}{U_{N2}} = \frac{10000}{400} = 25$$





$$Z_1 = \frac{U_1}{I_1}$$

Henføring af netimpedans og impedans af HVFL til 400 V niveau:

Faktor 1,5 x R på lavspændingskabler (Beregningseksempel)

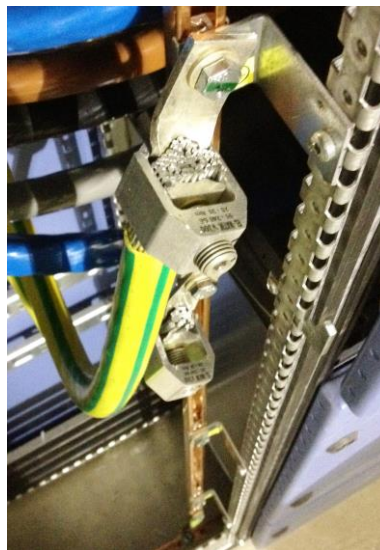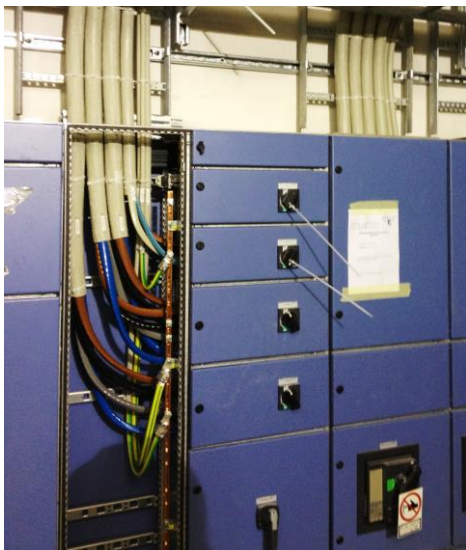- Opvarmning af leder er primær årsag til faktor 1,5
- Samlingsresistans i kabelmuffer o.l. er sekundær årsag til faktor 1,5



Kortslutningsstrømmene (Beregningseksempel)

Den 3 fasede kortslutningsstrøm i tavle -A.1:

Den 2 fasede kortslutningsstrøm i tavle -A.1:

Den 1 fasede kortslutningsstrøm i tavle -A.1:

Spændingsfaktor c

60909-0 © IEC:2001

– 11 –

1.3.15

voltage factor c

ratio between the equivalent voltage source and the nominal system voltage U_n divided by $\sqrt{3}$.

The values are given in table 1

NOTE The introduction of a voltage factor c is necessary for various reasons. These are:

- voltage variations depending on time and place,
- changing of transformer taps,
- neglecting loads and capacitances by calculations according to 2.3.1,
- the subtransient behaviour of generators and motors.

60909-0 © IEC:2001

– 21 –

Table 1 – Voltage factor c

Nominal voltage U_n	Voltage factor c for the calculation of	
	maximum short-circuit currents $c_{\max}^{1)}$	minimum short-circuit currents c_{\min}
Low voltage 100 V to 1 000 V (IEC 60038, table I)	1,05 ³⁾ 1,10 ⁴⁾	0,95
Medium voltage >1 kV to 35 kV (IEC 60038, table III)	1,10	1,00
High voltage²⁾ >35 kV (IEC 60038, table IV)		

¹⁾ $c_{\max}U_n$ should not exceed the highest voltage U_m for equipment of power systems.
²⁾ If no nominal voltage is defined $c_{\max}U_n = U_m$ or $c_{\min}U_n = 0,90 \times U_m$ should be applied.
³⁾ For low-voltage systems with a tolerance of +6 %, for example systems renamed from 380 V to 400 V.
⁴⁾ For low-voltage systems with a tolerance of +10 %.

← Tabel over spændingsfaktor c findes også i bog 6 side 28

Spændingsfaktor C (Beregningseksempel)

Den 3 fasede kortslutningsstrøm i tavle -A.1 med spændingsfaktor c:

$$I_{K3F \underline{max}} = \frac{U_n \cdot c}{\sqrt{3} \cdot (\bar{Z}'_{net} + \bar{Z}'_{HVFL} + \bar{Z}_T + \bar{Z}_{LVFL})} = \frac{400 \cdot 1,10}{\sqrt{3} \cdot 0,0248} = \underline{10,2 \text{ kA}}$$

3 faset KS uden c faktor:

$$I_{K3F \underline{min}} = \frac{U_n \cdot c}{\sqrt{3} \cdot (\bar{Z}'_{net} + \bar{Z}'_{HVFL} + \bar{Z}_T + \bar{Z}_{LVFL})} = \frac{400 \cdot 0,95}{\sqrt{3} \cdot 0,0248} = \underline{8,85 \text{ kA}}$$

$I_{K3F} = 9,29 \text{ kA}$

Den 2 fasede kortslutningsstrøm i tavle -A.1 med spændingsfaktor c:

$$I_{K2F \underline{max}} = \frac{U_n \cdot c}{2 \cdot (\bar{Z}'_{net} + \bar{Z}'_{HVFL} + \bar{Z}_T + \bar{Z}_{LVFL})} = \frac{400 \cdot 1,10}{2 \cdot 0,0248} = \underline{8,87 \text{ kA}}$$

2 faset KS uden c faktor:

$$I_{K2F \underline{min}} = \frac{U_n \cdot c}{2 \cdot (\bar{Z}'_{net} + \bar{Z}'_{HVFL} + \bar{Z}_T + \bar{Z}_{LVFL})} = \frac{400 \cdot 0,95}{2 \cdot 0,0248} = \underline{7,66 \text{ kA}}$$

$I_{K2F} = 8,05 \text{ kA}$

Den 1 fasede kortslutningsstrøm i tavle -A.1 med spændingsfaktor c:

$$I_{K1F \underline{max}} = \frac{U_n \cdot c}{\sqrt{3} \cdot (\bar{Z}'_{net} + \bar{Z}'_{HVFL} + \bar{Z}_T + 2 \cdot \bar{Z}_{LVFL})} = \frac{400 \cdot 1,10}{\sqrt{3} \cdot 0,0395} = \underline{6,43 \text{ kA}}$$

1 faset KS uden c faktor:

$$I_{K1F \underline{min}} = \frac{U_n \cdot c}{\sqrt{3} \cdot (\bar{Z}'_{net} + \bar{Z}'_{HVFL} + \bar{Z}_T + 2 \cdot \bar{Z}_{LVFL})} = \frac{400 \cdot 0,95}{\sqrt{3} \cdot 0,0395} = \underline{5,55 \text{ kA}}$$

$I_{K1F} = 5,85 \text{ kA}$